

ECE 272 Lab 2
Fall 2018

Adders on an FPGA
Phi Luu

October 8th, 2018
Grading TA: Edgar Perez
Lab Partner: Benjamin Geyer

1 Introduction

This lab focuses on the logic level of computer arithmetic and a critical component of processors—called the *Arithmetic Logic Unit* (ALU)—that performs arithmetic operations. This lab shows how to implement a system of adders to perform and demonstrate additions of two 4-bit binary numbers using combinational logic design.

There are three main ways of implementing multi-bit adders from combinational logic: ripple-carry, carry-lookahead, and carry-save. There is a tradeoff between speed and size of the three methods. Ripple-carry adders are the slowest but smallest, and carry-save adders are the fastest but biggest. The logic designer can choose between the three depending on the situation. Because the ripple-carry adder is easy to understand and implement, it will be the main focus on this lab.

We will also learn how to use Quartus Prime to design a ripple-carry adder from scratch (logic gates and wires), make the adder itself as a logic symbol, and then use that symbol to perform 4-bit binary addition operations.

2 Design

A ripple-carry takes in three inputs—**operand1**, **operand2**, and the **carry-in**—and produces two outputs, the **sum** and the **carry-out**, as sketched in Figure 1 below:

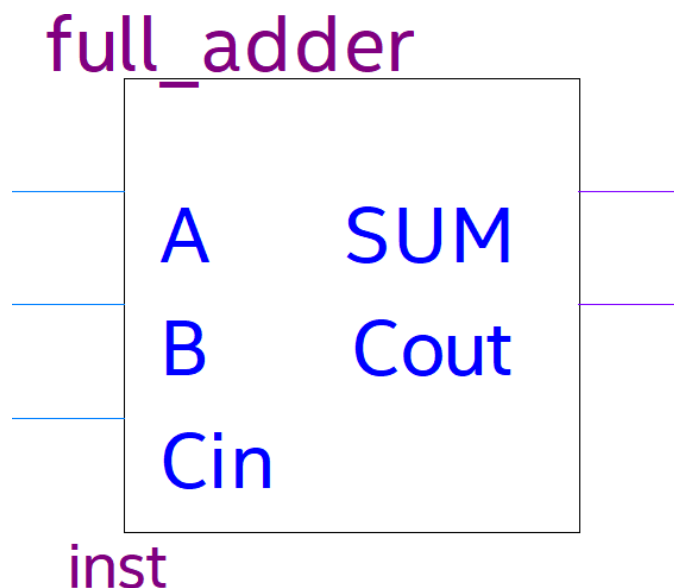


Figure 1: The pin layout of a full ripple-carry adder for $A + B$

The carry-in works similarly to when we carry the numbers when adding decimals together. If the value of the carry-in is 1, then the addition on the more significant column will increase by 1. If the next column's addition result is already 1 before adding the carry-in, then its value will circle back to 0 and continue carrying the 1 to the more significant column and so on.

The block diagram showing the structure of the implementation is as follows:

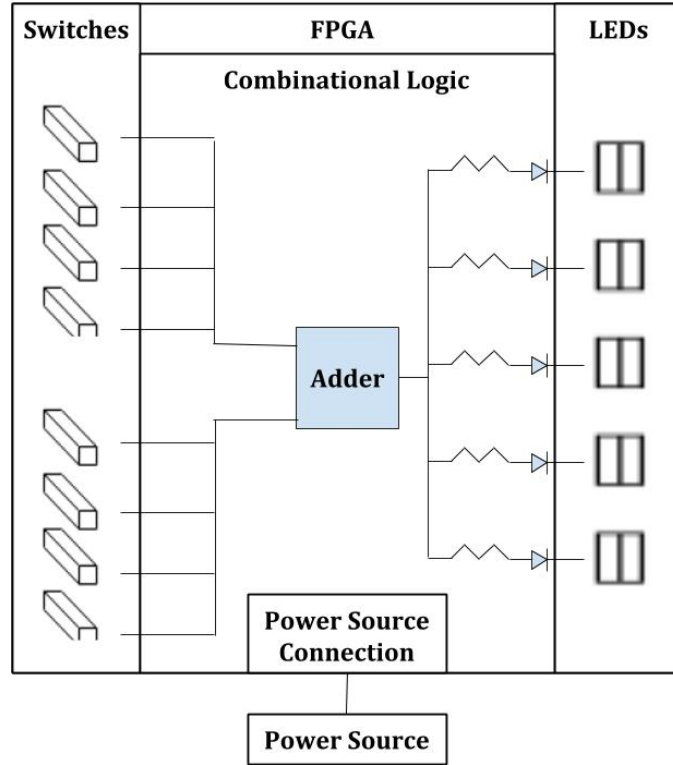


Figure 2: The block diagram showing the connections between the switches, the FPGA, and the LEDs in a 4-bit binary adder implementation

Since the circuit takes in two 4-bit binary numbers as operands, there are four pairs of 2-bit inputs—one bit from the first operand and the other from the second operand. Each ripple-carry adder will take in one of the pairs described earlier and return the carry-out with the sum. The adder that ties to the addition of the **least significant** bits of the two binary numbers will have **no carry-in value** ($C_{in0} = 0$). Similarly, the adder that ties to the addition of the **most significant** bits of the two binary numbers will have its **carry-out connected to the output**, as in some cases the result can be a 5-bit binary number. Finally, the remaining adders will connect to each other in the same way as follows: **the carry-out of the less significant adders connects to the carry-in of the more significant adders**.

A picture is worth a thousand words. Therefore, the schematic of the internal structure of a ripple-carry adder and the schematic of the 4-bit binary addition circuit are shown in Figures 3 and 4, respectively.

Using Figure 3, the sum SUM and the carry-out C_{out} of a ripple-adder with operand A , operand B , and carry-in C_{in} are expressed in the following sum-of-products forms in Equations 1 and 2:

$$SUM = A \oplus B \oplus C_{in} \quad (1)$$

$$C_{out} = AB + AC_{in} \oplus BC_{in} \quad (2)$$

A full-adder truth table used when adding two binary digit is shown in Table 1. Extending this table to construct a partial 4-bit adder truth table (Table 2), we obtain the following results:

Operand1	+	Operand2	+	Carry In	=	Value (2-bit Binary)	Value (Unsigned Decimal)
0b0	+	0b0	+	0b0	=	0b00	0
0b0	+	0b0	+	0b1	=	0b01	1
0b0	+	0b1	+	0b0	=	0b01	1
0b0	+	0b1	+	0b1	=	0b10	2
0b1	+	0b0	+	0b0	=	0b01	1
0b1	+	0b0	+	0b1	=	0b10	2
0b1	+	0b1	+	0b0	=	0b10	2
0b1	+	0b1	+	0b1	=	0b11	3

Table 1: A full-adder truth table

Operand1	+	Operand2	=	Value (5-bit Binary)	Value (Unsigned Decimal)	Value (Hexadecimal)
0b0000	+	0b0000	=	0b00000	0	0x00
0b0000	+	0b0001	=	0b00001	1	0x01
0b0000	+	0b0010	=	0b00010	2	0x02
0b0000	+	0b0011	=	0b00011	3	0x03
0b0000	+	0b0100	=	0b00100	4	0x04
0b0000	+	0b0101	=	0b00101	5	0x05
0b1000	+	0b0000	=	0b01000	8	0x08
0b1000	+	0b0001	=	0b01001	9	0x09
0b1000	+	0b0010	=	0b01010	10	0x0A
0b1000	+	0b0011	=	0b01011	11	0x0B
0b1111	+	0b0011	=	0b10010	18	0x12
0b1111	+	0b1000	=	0b10111	23	0x17
0b1111	+	0b1010	=	0b11001	25	0x19
0b1111	+	0b1011	=	0b11010	26	0x1A

Table 2: A partial 4-bit adder truth table

3 Results

Before uploading the project to the real FPGA, we created a simulation waveform of the addition. Specifically, from Table 2 we picked **0b0000 + 0b0000** (first row), **0b0000 + 0b0100** (fifth row), **0b1000 + 0b0011** (tenth row), and **0b1111 + 0b1010** (thirteenth row) and tested them in the simulation. Figure 5 shows the simulation result:

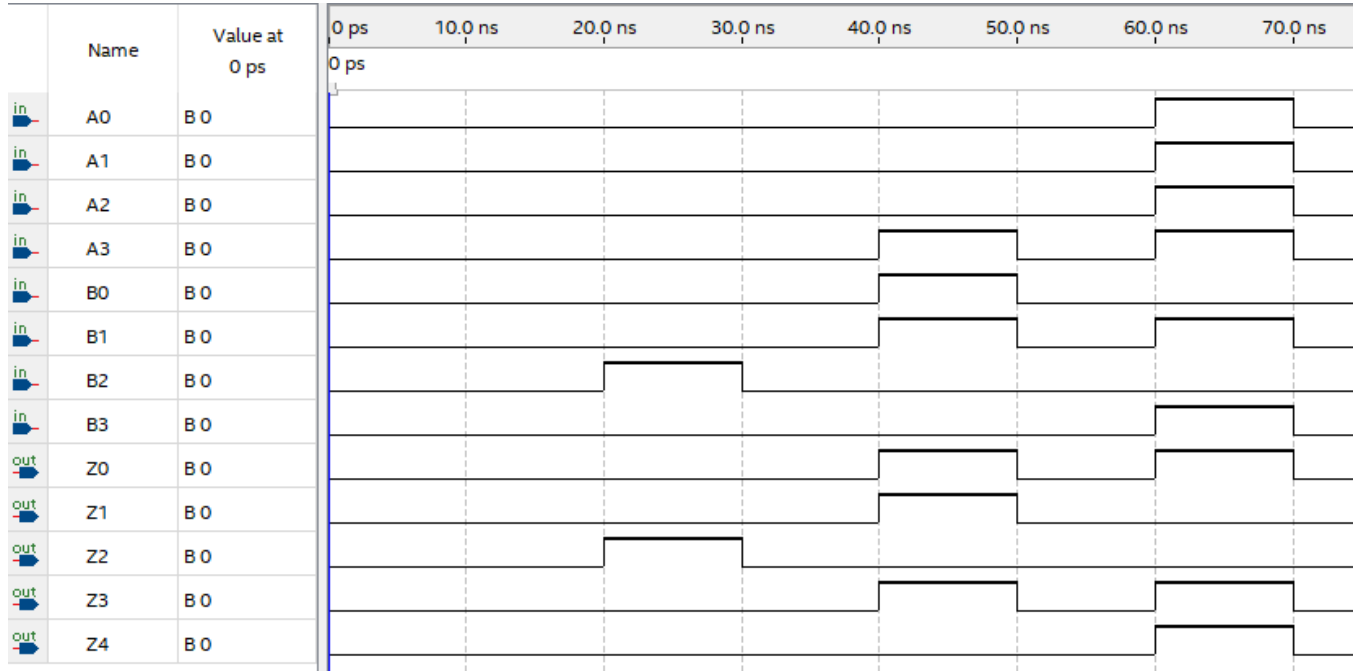


Figure 5: Simulation results after testing first (0 - 10ns), fifth (20ns - 30ns), tenth (40ns - 50ns), and thirteenth (60ns - 70ns) rows of Table 2

The simulation yielded **0b0000 + 0b0000 = 0b000000**, **0b0000 + 0b0100 = 0b00100**, **0b1000 + 0b0011 = 0b01011**, **0b1111 + 0b1010 = 0b11001**, which matched with the corresponding results calculated from Table 2. We then moved on to real-board testing and also got the same results. Based on the results, we hence believed that our implementations of the 4-bit binary adders were correct.

4 Experiment Notes

Reflection

This lab brought us from simple schematic design of lab 1 to a more complex design, where we had to define our own ripple-carry adders from scratch (logic gates and wires) and then used the adders in our main circuit. This was quite a big change, but we were able to grasp the idea of reusing sub-circuits and successfully made the grand system work. We are looking forward to more challenging labs in the future.

Study Questions

1. Explain how you would convert your 4-bit adder to a 4-bit adder/subtractor.

Subtraction in decimal system is the same as addition with the opposite of the second operand: $A_{10} - B_{10} = A_{10} + (-B_{10})$. Similarly, we can subtract a binary number B_2 from A_2 by adding A_2 with the two's complement of B_2 : $A_2 - B_2 = A_2 + (-B_2)$. Therefore, add an inverter to every bit of B before it goes to a logic gate, and we will have a 4-bit subtractor.

2. In your own words, explain what pull resistors do in the FPGA.

The pull-up and pull-down setups of a circuit should have a switch in it. For example, a pull-up resistor setup means a resistor ties the input pin of the FPGA to V_{CC} and a switch connecting the circuit to GND. Similarly, a pull-down resistor setup means a resistor ties the input pin of the FPGA to GND and a switch connecting the circuit to V_{CC} . See Figure 6 below

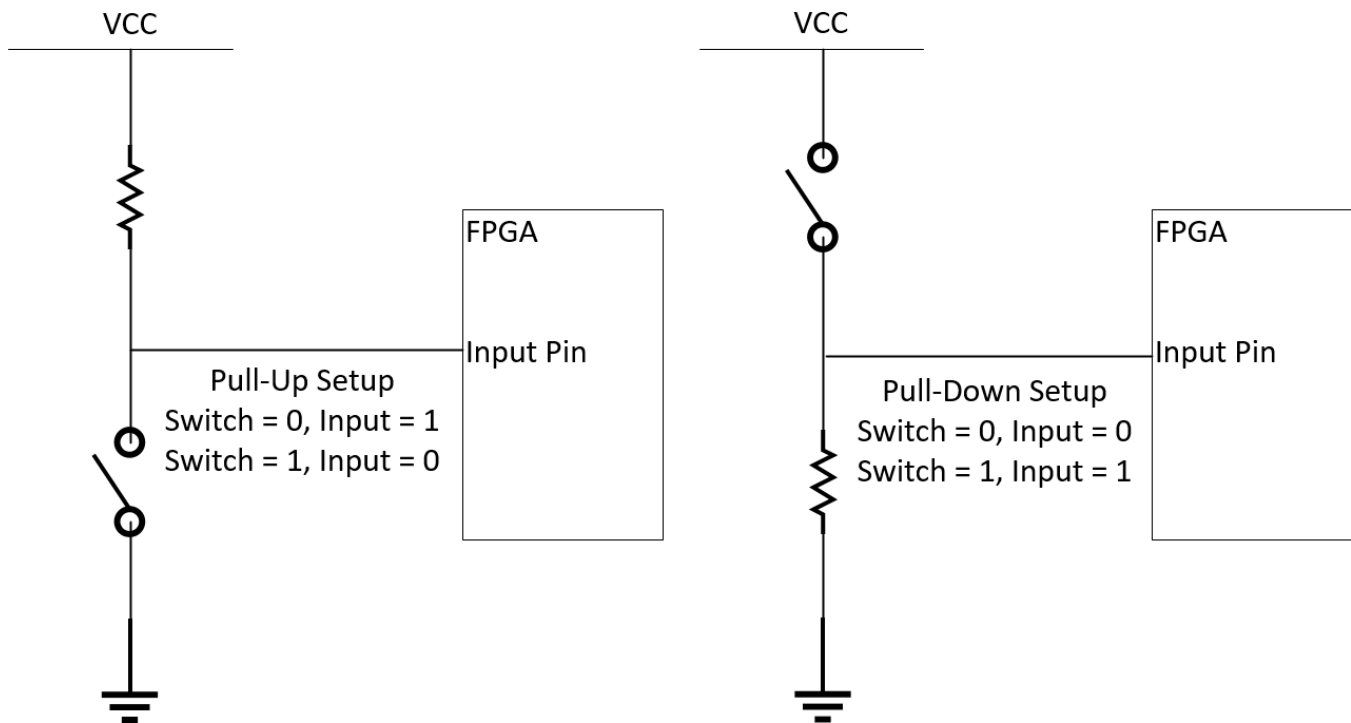


Figure 6: Pull-up and pull-down resistor setups and their truth tables

The outcome is different between the two setups. However, a significant thing here is that by using pull resistors, we effectively make sure that the input *always* receives *either 0 or 1—nothing in between and thus no floating value*. The resistors significantly reduce the noise the input pin of the FPGA would take and guarantee the FPGA would never take a floating value as an input.

3. Explain your selection for the pullmode for the pin connected to the least-significant full-adder's carry-in.

We pulled least-significant full-adder's carry-in to GND because when we add the very first bits of the two binary numbers together, there is always no initial carry-in (or $C_{in0} = 0$).

Appendix

No appendix is available in this lab.