

ECE 272 Lab 3
Fall 2018

Combinational Logic (Seven-Segment Driver)
Phi Luu

October 24th, 2018
Grading TA: Edgar Perez
Lab Partner: Benjamin Geyer

1 Introduction

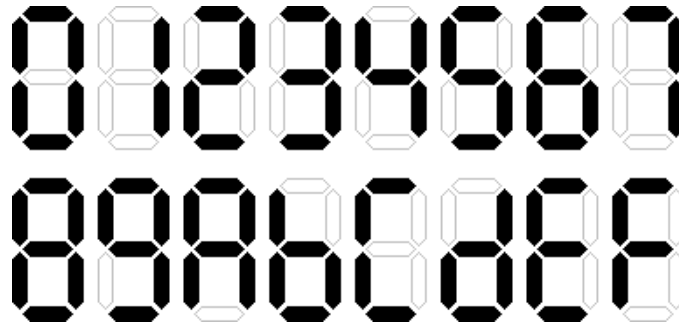


Figure 1: Seven-segment display showing hexadecimal digits [1]

2 Design

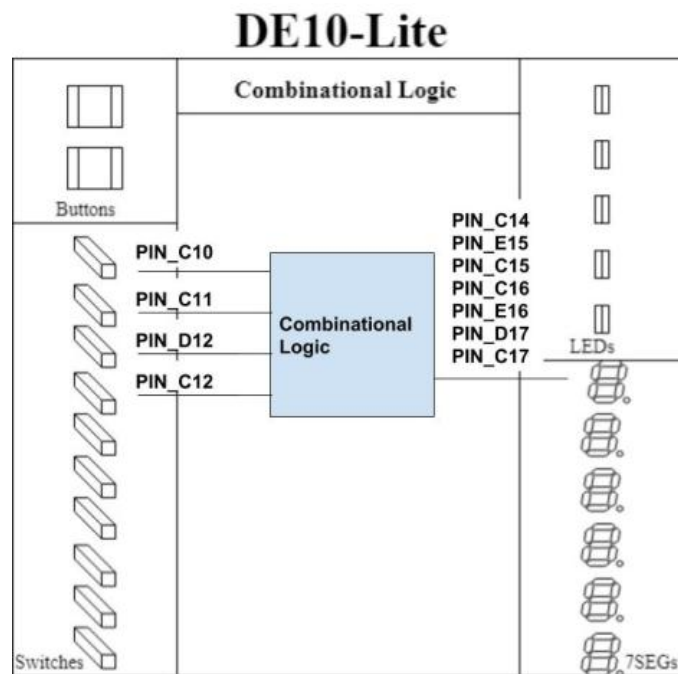


Figure 2: Block diagram

Seg_A

AB \ CD	00	01	11	10
00	0	1	0	0
01	1	0	1	0
11	0	0	0	1
10	0	0	0	0

$$Seg_A = \overline{A}BCD + \overline{A}B\overline{C}\overline{D} + ABCD + \overline{A}BC\overline{D}$$

Seg_B

AB \ CD	00	01	11	10
00	0	0	1	0
01	0	1	0	0
11	0	0	1	1
10	0	1	1	0

$$Seg_B = B\overline{C}\overline{D} + ACD + ABD + \overline{A}B\overline{C}\overline{D}$$

Seg_C

AB \ CD	00	01	11	10
00	0	0	1	0
01	0	0	0	0
11	0	0	1	0
10	1	0	1	0

$$Seg_C = ABC + ABD + \overline{A}B\overline{C}\overline{D}$$

Seg_D

AB \ CD	00	01	11	10
00	0	1	0	0
01	1	0	0	0
11	0	1	1	0
10	0	0	0	1

$$Seg_D = BCD + \overline{A}B\overline{C}\overline{D} + \overline{A}BC\overline{D} + \overline{A}B\overline{C}D$$

Seg_E

AB \ CD	00	01	11	10
00	0	1	0	0
01	1	1	0	1
11	1	1	0	0
10	0	0	0	0

$$Seg_E = \overline{A}D + \overline{A}BC + \overline{B}C\overline{D}$$

Seg_F

AB \ CD	00	01	11	10
00	0	0	0	0
01	1	0	1	0
11	1	1	0	0
10	1	0	0	0

$$Seg_F = \overline{A}CD + \overline{A}BD + \overline{A}BC + \overline{A}BCD$$

Seg_G

AB \ CD	00	01	11	10
00	1	0	1	0
01	1	0	0	0
11	0	1	0	0
10	0	0	0	0

$$Seg_G = \overline{A}BC + \overline{A}BCD + \overline{A}BC\overline{D}$$

Input (Hexadecimal)	Input (4-bit Binary)	Seg _A	Seg _B	Seg _C	Seg _D	Seg _E	Seg _F	Seg _G
0	0000	0	0	0	0	0	0	1
1	0001	1	0	0	1	1	1	1
2	0010	0	0	1	0	0	1	0
3	0011	0	0	0	0	1	1	0
4	0100	1	0	0	1	1	0	0
5	0101	0	1	0	0	1	0	0
6	0110	0	1	0	0	0	0	0
7	0111	0	0	0	1	1	1	1
8	1000	0	0	0	0	0	0	0
9	1001	0	0	0	0	1	0	0
a	1010	0	0	0	1	0	0	0
b	1011	1	1	0	0	0	0	0
c	1100	0	1	1	0	0	0	1
d	1101	1	0	0	0	0	1	0
e	1110	0	1	1	0	0	0	0
f	1111	0	1	1	1	0	0	0

Table 1: Conversion table between hexadecimal, 4-bit binary, and seven-segment decoder

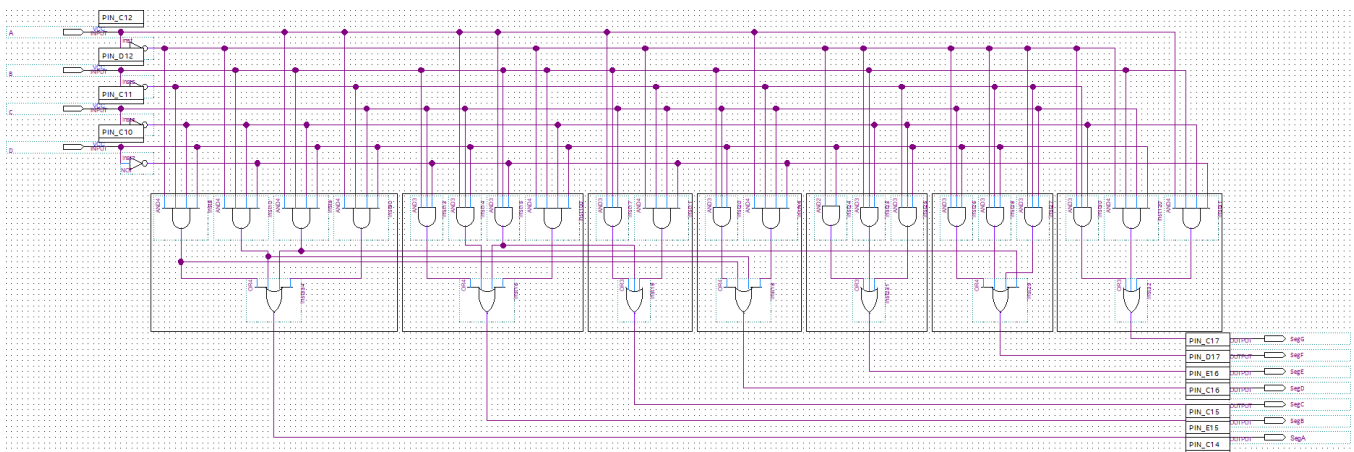


Figure 3: A schematic for the seven-segment display decoder. Due to the large difference between the size of the schematic and the available space, an image with higher resolution has been uploaded [here](#).

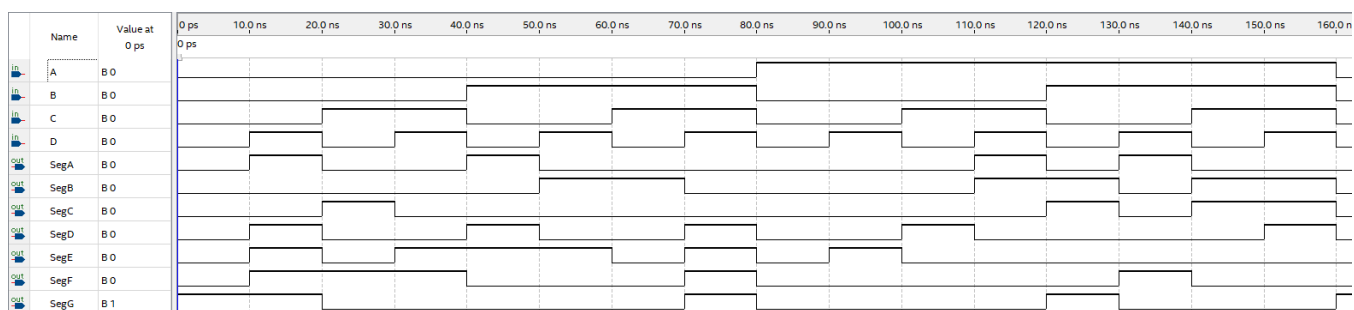


Figure 4: Simulation waveform of the program with each 10-nanosecond interval representing a hexadecimal digit

3 Results

4 Experiment Notes

Reflection

Study Questions

1. When is a simulation necessary? Was it useful for this section?

Appendix

No appendix is available in this lab.

References

- [1] E. E. S. Exchange, “Hex to 7 segment decoder for a common anode 7 seg display.” <https://electronics.stackexchange.com/questions/373034/hex-to-7-segment-decoder-for-a-common-anode-7-seg-display>, 2018.