

EXAMPLE PROBLEMS

Example 3.1: How many transistors are needed to build the D flip-flop described in this section?


Device	Number of transistors
2-input NAND/NOR	4
NOT	2
2-input AND/OR	6 (NAND/NOR + NOT)
SR latch	8 ($2 \times \text{NOR}$)
D latch	22 (SR latch + $2 \times \text{AND}$ + NOT)
D flip-flop	46 ($2 \times \text{D latch}$ + NOT)

Variation: How many transistors are needed to build an enabled flip-flop?

An enabled flip-flop uses a D flip-flop and a 2-input AND gate.

Thus, an enabled flip-flop requires 52 transistors

 
Example 3.2: Determine output Q from the waveforms of CLK and D



Variation: Same graph as above but with an enabled flip-flop



Example 3.6 : FSM state encoding

 


current state	next state
S0	S1
S1	S2
S2	S0

State	$S_1:0$
S0	00
S1	01
S2	10

current state	output
S0	1
S1	0
S2	0


State transition table with binary encoding

current state		next state		Output
S_1	S_0	S_1'	S_0'	Y
0	0	0	1	1
0	1	1	0	0
1	0	0	0	0
 
$$\Rightarrow \begin{cases} S_1' = \overline{S_1} S_0 \\ S_0' = \overline{S_1} \overline{S_0} \\ Y = \overline{S_1} \overline{S_0} \end{cases}$$


State transition table with one-hot encoding

Current state			Next state		
S_2	S_1	S_0	S_2'	S_1'	S_0'
0	0	1	0	1	0
0	1	0	1	0	0
1	0	0	0	0	1
 
$$\begin{cases} S_2' = S_1 \\ S_1' = S_0 \\ S_0' = S_2 \\ Y = S_0 \end{cases}$$


Variation:
Reset



State	binary encoding
State	$S_1:0$
S0	00
S1	01
S2	10


output table:	
current state	output
S0	0
S1	1
S2	1

State transition table with binary encoding


current state		next state		output
S_1	S_0	S'_1	S'_0	Y
0	0	0	1	0
0	1	1	0	1
1	0	0	0	1

$$\Rightarrow \begin{cases} S'_1 = \bar{S}_1 S_0 \\ S'_0 = \bar{S}_1 \bar{S}_0 \\ Y = \bar{S}_1 S_0 + S_1 \bar{S}_0 \end{cases}$$

Sketch:

 

Example 3.3: Astable circuits

 

Suppose $X_{init} = 0$. Then, $Y = 1$ and $Z = 0$, but then $X = 1$.

Suppose $X_{init} = 1$. Then, $Y = 0$ and $Z = 1$, but then $X = 0$.

The circuit has no stable state (astable circuit)

X , Y , and Z will oscillate between 0 and 1



is this circuit stable or astable?

Truth table:

S	R	\bar{S}	\bar{R}	N1	N2	Q_{prev}	Q	\bar{Q}
0	0	1	1	0	1	0	0	1
0	1	1	0	0	1	X	0	1
1	0	0	1	1	0	X	1	0
1	1	0	0	1	1	X	1	1

 \Rightarrow Stable sequential circuitExample 3.10: Timing Analysis $t_{pcq} = 80\text{ps}$, $t_{setup} = 50\text{ps}$, $t_{pd} = 40\text{ps}$, 3 logic gates. $f_{cmax} = ?$ Minimum clock cycle $= T_{cmin} = t_{pcq} + 3t_{pd} + t_{setup} = 250\text{ps}$ Maximum clock frequency $= f_{cmax} = \frac{1}{T_{cmin}} = 4\text{GHz}$ Variation: $t_{pcq} = 75\text{ps}$, $t_{setup} = 10\text{ps}$, $t_{pd} = 100\text{ps}$, 7 logic gates. $f_{cmax} = ?$ Minimum clock cycle $= T_{cmin} = t_{pcq} + 7t_{pd} + t_{setup} = 785\text{ps}$ Maximum clock frequency $= f_{cmax} = \frac{1}{T_{cmin}} = 1.274\text{GHz}$